

(*) Loading of Lines

- * For Distortionless Line $RC = LG$ is the Condition to be satisfied.
- * For practical Tx line, $\frac{R}{G} \gg \frac{L}{C}$, hence the signal is distorted.
∴ To satisfy the condition, it is necessary to reduce $\frac{R}{G}$ or to increase $\frac{L}{C}$.
- * R can be decreased by increasing the area of cross section i.e.) diameter of the conductor. This increases the size/cost of the line.
- * G can be increased by using poor insulators. that is easy & economical.
 $G \uparrow$ the leakage of signal will increase thus received signal will become weak that signal should be amplified at intermediate stage. This makes the design complicated.
- * Hence this possibility is ruled out in practice.
- * ∴ it is necessary to increase $\frac{L}{C}$ ratio to achieve distortionless line.
- * it is allowed to increase L (or) decrease C .
- * if C is to be reduced, then the separation b/w two lines are more.

- * Thus the brackets will now carry less number of wires due to increased separation.
- * The line will become very much costlier. hence this possibility also ruled out.
- * Only choice is increasing 'L'

This opted in practice.

⇒ The process of increasing the inductance (L) of a line artificially i.e.) lumped inductors were spaced at regular intervals along the line. This use to achieve distortionless line is called "Loading of line".

Types of loading:

1) Continuous Loading: / Krump loading / Heavy side.

In this type of loading, a type of iron or magnetic material such as permalloy (or) μ -metal having high permeability are wound round the conductor to be loaded.


* If μ of the surrounding medium increase, thereby inductance (L) increases.

* This method increases the inductances upto 65 mH/km , but expensive in construction.

* Eddy current & hysteresis losses in magnetic material increase the primary constant (R).

*. Suppose if there is a small difference in mechanical treatment (or) pressure b/w the tape & conductor that cause large variations in primary constants.

*.

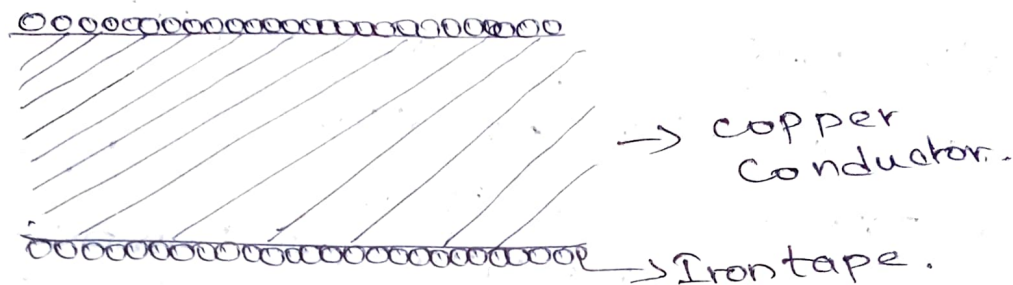

* continuous loading used only in ocean cables where the problem of making water tight joints at loading points makes lapped loading difficult.

* Adv:

The α increases uniformly with increase in frequency.

propagation constant of continuous loaded cable

* for continuous loaded cable it is assumed that $[G \ll \omega C]$ & L is increased such that:

$$\boxed{\omega L \gg R}$$

w.k.T

$$Z = R + j\omega L \quad ; \quad Y = \cancel{G} + j\omega C = j\omega C.$$

①

$$\begin{aligned}
 \varphi &= \sqrt{ZY} = \sqrt{(R + j\omega L)(j\omega C)} \\
 &= \sqrt{\sqrt{R^2 + \omega^2 L^2} \left[\tan^{-1}\left(\frac{\omega L}{R}\right) \times \omega C \right] \frac{\pi}{2}} \quad \xrightarrow{\sqrt{\omega^2 C^2}} \\
 &= \sqrt{\omega^2 L \sqrt{1 + \frac{R^2}{\omega^2 L^2}} \times \omega C \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right) + \frac{\pi}{2} \right]}
 \end{aligned}$$

$$\varphi = \sqrt{\omega^2 LC \sqrt{1 + \frac{R^2}{\omega^2 L^2}} \left[\pi - \tan^{-1}\left(\frac{R}{\omega L}\right) \right]} \quad \text{--- (2)}$$

$$\therefore \boxed{\omega L \gg R}$$

$$\varphi = \sqrt{\omega^2 LC \left[\pi - \tan^{-1}\left(\frac{R}{\omega L}\right) \right]}$$

$$\varphi = \omega \sqrt{LC} \left[\frac{\pi}{2} - \frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right) \right] \quad \text{--- (3)}$$

$$\text{here } \theta = \frac{\pi}{2} - \frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right) \quad \text{--- (4)}$$

$$\cos \theta = \cos \left[\frac{\pi}{2} - \frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right) \right]$$

$$\begin{aligned}
 &= \sin \left[\frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right) \right] \quad \left[\because \text{for smaller angle} \right. \\
 &= \sin \left[\frac{1}{2} \frac{R}{\omega L} \right] \quad \left. \begin{aligned} \tan^{-1} \theta &= \theta \\ \sin \theta &= \theta \end{aligned} \right]
 \end{aligned}$$

$$\boxed{\cos \theta = \frac{R}{2\omega L}} \quad \text{--- (5)}$$

$$\sin \theta = \sin \left[\frac{\pi}{2} - \frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right) \right] \quad \because \omega L \gg R$$

$$\boxed{\sin \theta = \sin \frac{\pi}{2} = 1} \quad \text{--- (6)}$$

from (3)

$$V = \omega \sqrt{LC} \angle \theta = \omega \sqrt{LC} e^{j\theta}$$

$$= \omega \sqrt{LC} [\cos \theta + j \sin \theta]$$

$$V = \omega \sqrt{LC} \left[\frac{R}{2\omega L} + j \right]$$

$$\alpha + j\beta = \frac{R}{2} \sqrt{\frac{C}{L}} + j\omega \sqrt{LC}$$

Comparing real & imaginary

$$\boxed{\alpha = \frac{R}{2} \sqrt{\frac{C}{L}}} \quad ; \quad \boxed{\beta = \omega \sqrt{LC}}$$

$$V_p = \frac{V}{\beta} = \frac{V}{\omega \sqrt{LC}} \quad \therefore \boxed{V_p = \frac{1}{\sqrt{LC}}}$$


under the assumption; $G=0$ & $\omega L \gg R$,
 α & V_p both are independent of frequency &
the loaded cable will be distortionless.

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$; \quad \omega L \gg R, \quad G=0$$

$$Z_0 = \sqrt{\frac{j\omega L}{j\omega C}}$$

$$\boxed{Z_0 = \sqrt{\frac{L}{C}}}$$

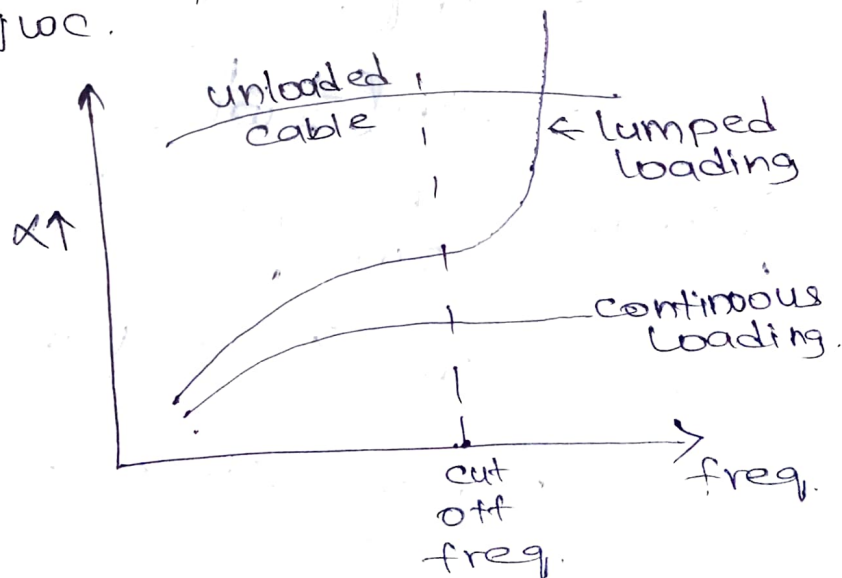

Advantage:

- α is independent of frequency.
- α is decreased by increasing L provided R is not increased.
- Increase in L upto 100 mh/unit length is possible

Dis Adv:

- Very Expensive.
- Existing lines cannot be modified by this method, only replacement is possible.
- Here it achieves only small increase in L /unit length.

ii) Lumped Loading:

- * In this type of loading, the inductors are introduced in lumps at uniform distance in the line, which is in the form of coils called lumped loading.
- * The inductors are introduced in both the lines to keep the line a balanced circuit.
- * It behaves as LPF.
- * It is more convenient than continuous loading provided that the frequency is limited to cut off frequency.

* The loading coils have certain resistance
thus $L \uparrow R$ also increases.


* If $R \uparrow$ then hysteresis & eddy current losses
in loading coil & hence distortion increases in line.

$$f_c = \frac{1}{\pi \sqrt{L_c C d}}$$

$L_c \rightarrow$ inductance of the loading coil & cable/km.

$C \rightarrow$ capacitance /km.

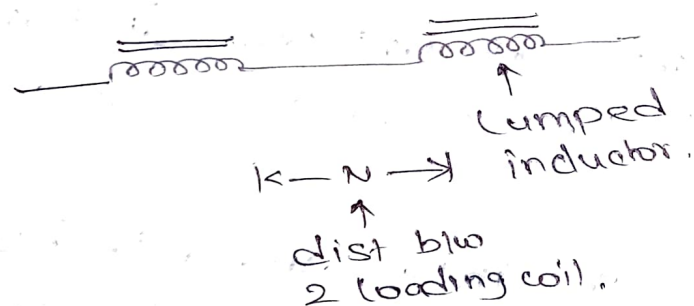$d \rightarrow$ distance b/w two conductors.



propagation constant of lumped loaded cable.

(or)


Campbell's formula.

* The performance of a line loaded at uniform intervals can be obtained by considering a symmetrical section of line from the center of

one loading coil to the center of the next, where the loading coil impedance is Z_0 .

GA Campbell developed a formula for propagation constant α of loaded line in terms of secondary constant of unloaded line & the impedance of loading coil Z_0 .

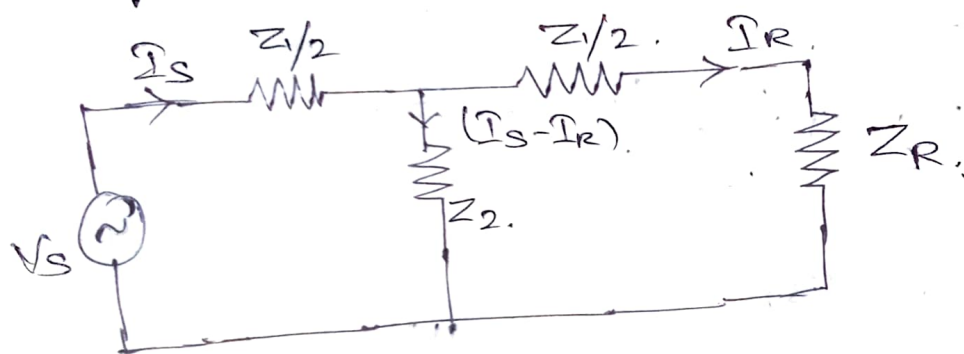Equivalent T-N/w of unloaded line as shown.



The equation Voltage & current at any point in a line in terms of sending end voltage & current (V_s & I_s) is given by.

$$V = V_s \cosh \alpha x - I_s Z_0 \sinh \alpha x.$$

$$I = I_s \cosh \alpha x - \frac{V_s}{Z_0} \sinh \alpha x.$$

$x \rightarrow$ distance measured from the sending end.

* At the receiving end; $x = L$, $V = V_R$, $I = I_R$.

$$V_R = V_s \cosh \alpha L - I_s Z_0 \sinh \alpha L; \quad \text{--- (1)}$$

$$I_R = I_s \cosh \alpha L - \frac{V_s}{Z_0} \sinh \alpha L. \quad \text{--- (2)}$$

Apply Kirchhoff's KVL to equivalent T-nb.

$$V_S = I_S \frac{Z_1}{2} + Z_2 (I_S - I_R)$$

$$V_S = I_S \left[\frac{Z_1}{2} + Z_2 \right] - I_R Z_2$$

$$I_R Z_2 = I_S \left[\frac{Z_1}{2} + Z_2 \right] - V_S$$

$$I_R = \frac{I_S}{Z_2} \left[\frac{Z_1}{2} + Z_2 \right] - \frac{V_S}{Z_2}$$

$$I_R = I_S \left[\frac{Z_1}{2Z_2} + 1 \right] - \frac{V_S}{Z_2} \quad \text{--- (3)}$$

Comparing (2) & (3).

$$\frac{Z_1}{2Z_2} + 1 = \cosh \theta l$$


$$\frac{Z_1}{2Z_2} = \cosh \theta l - 1$$

$$\frac{Z_1}{2} = \frac{Z_0}{\sinh \theta l} [\cosh \theta l - 1]$$

Similarly

$$\frac{1}{Z_2} = \frac{\sinh \theta l}{Z_0}$$

$$Z_2 = \frac{Z_0}{\sinh \theta l}$$

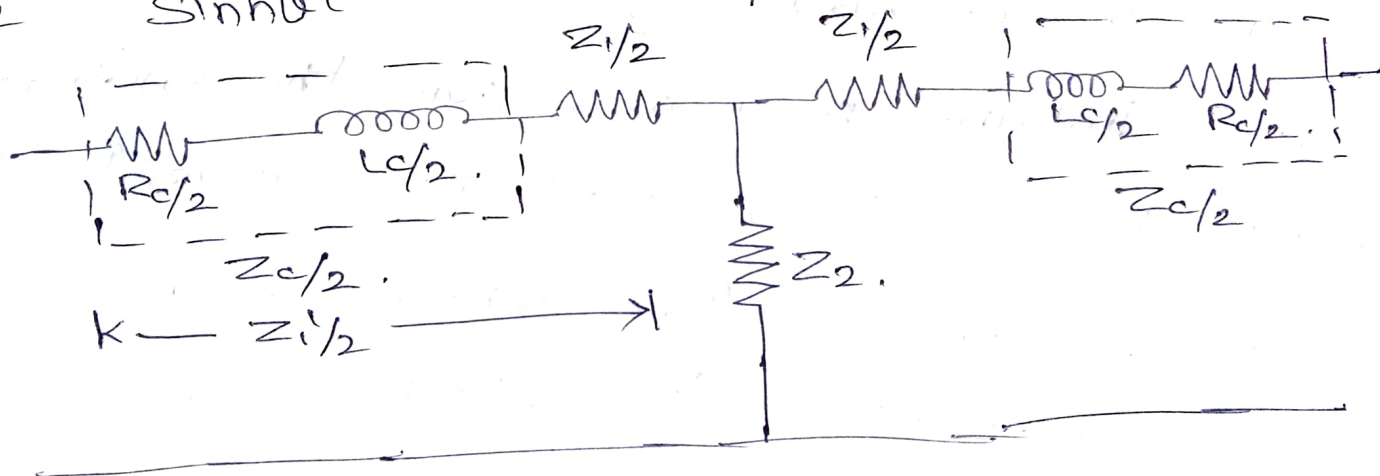

Z_1 & Z_2 are Series & Shunt arm impedance of unloaded line.

from fig; $\frac{Z_1'}{2} = \frac{Z_c}{2} + \frac{Z_1}{2} = \frac{Z_c}{2} + \frac{Z_0}{\sinh \ell}$

Equivalent T-n/w of loaded ~~unloaded~~ line is represented.

$Z_c \rightarrow$ impedance of loading coil.

$d \rightarrow$ distance b/w centre of two coils.

$Z_1, Z_2 \rightarrow$ impedance of unloaded line.

\therefore The receiving current I_R in terms of V_S, I_S of loaded line is.

$$I_R = I_S \cosh \ell - \frac{V_S}{Z_0} \sinh \ell. \quad \text{--- (4)}$$

Apply KVL.

$$V_S = I_S \left[\frac{Z_c}{2} + \frac{Z_1}{2} \right] + [I_S - I_R] Z_2$$

$$V_S = I_S \left[\frac{Z_c}{2} + \frac{Z_1}{2} + Z_2 \right] - I_R Z_2$$

$$I_R Z_2 = I_S \left[\frac{Z_c}{2} + \frac{Z_1}{2} + Z_2 \right] - V_S$$

$$I_R = \frac{I_S}{Z_2} \left[\frac{Z_c}{2} + \frac{Z_1}{2} + Z_2 \right] - \frac{V_S}{Z_2}$$


$$I_R = I_S \left[\frac{Z_c}{2Z_2} + \frac{Z_1}{2Z_2} + 1 \right] - \frac{V_S}{Z_2} \quad \text{--- (5)}$$

Comparing (4) & (5) we get,

$$\frac{Z_c}{2Z_2} + \frac{Z_1}{2Z_2} + 1 = \cosh \ell$$

$$\frac{1}{Z_2} = \frac{\sinh \ell}{Z_0}$$

$$\boxed{Z_2 = \frac{Z_0}{\sinh \ell}}$$

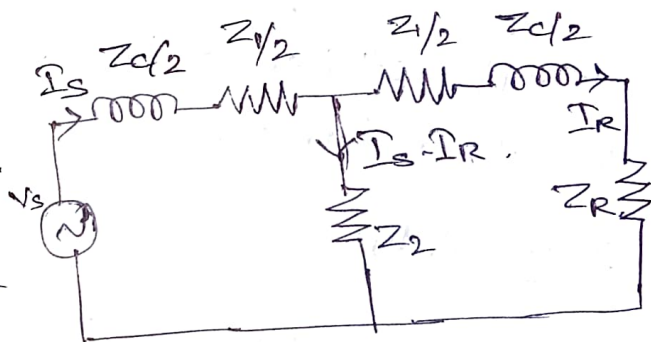

$$1 + \frac{Z_1 + Z_0}{2Z_2} = \cosh \theta_d = 1 + \frac{\frac{Z_1 + Z_0}{2}}{Z_2} = 1 + \frac{Z_1}{2Z_2}$$

Sub Z_2 & Z_0 , Z_1 , of unloaded

$$\cosh \theta_d = 1 + \frac{\frac{Z_0(\cosh \theta_d - 1)}{\sinh \theta_d}}{\frac{Z_0}{\sinh \theta_d}} + \frac{Z_1}{2Z_0/\sinh \theta_d}$$

$$\cosh \theta_d = \cancel{1} + \cosh \theta_d - \cancel{1} + \frac{Z_1 \sinh \theta_d}{2Z_0}$$

$$\cosh \theta_d = \cosh \theta_d + \frac{Z_1 \sinh \theta_d}{2Z_0}$$

* This eqn! makes the calculation of loading coil effects in reducing attenuation & distortion in the line.

Dis Adv:

- for a cable, Z_2 is essentially capacitive.
- Lpf = cable capacitance + lumped inductance.
- $f < f_c \rightarrow$ Attenuation is reduced.
- $f > f_c \Rightarrow$ Attenuation rises.

Adv:

- * cost is less.
- * existing lines can be modified.
- * Inductance is not increased with a limited value.

===== x ===== x =====